

## CS224 Lab 4 Preliminary Report Section-1 Ata Seren 21901575

Part 1.a

Location of Instruction (hex)	Machine Instruction (hex)	Assembly Language Equivalent			
00	20020005	addi \$v0, \$0, 5			
04	2003000c	addi \$v1, \$0, 12			
08	2067fff7	addi \$a3, \$v1, 65527			
0c	00e22025	or \$a0, \$a3, \$v0			
10	00642824	and \$a1, \$v1, \$a0			
14	00a42820	add \$a1, \$a1, \$a0			
18	10a7000a	beq \$a1, \$a3, 10			
1c	0064202a	slt \$a0, \$v1, \$a0			
20	10800001	beq \$a0, \$0, 1			
24	20050000	addi \$a1, \$0, 0			
28	00e2202a	slt \$a0, \$a3, \$v0			
2c	00853820	add \$a3, \$a0, \$a1			
30	00e23822	sub \$a3, \$a3, \$v0			
34	ac670044	sw \$a3, 68(\$v1)			
38	8c020050	lw \$v0, 80(\$0)			
3c	08000010	j 3			
40	001f6020	add \$t4, \$0, \$ra			
44	0c000012	jal 18			
48	ac020054	sw \$v0, 84(\$0)			
4c	00039042	srl \$s2, \$v1, 1			
50	03e00008	jr \$ra			

 Part 1.e (I separated my waveform to make it visible)



 

## Part 1.f


- i) Writedata corresponds to value in destination register (rd in instruction).
- ii) If destination register isn't used and saved a data by an instruction before, writedata becomes undefined in waveform.
- iii) Readdata is mostly undefined because no data is read from memory to store or load in undefined parts.
- iv) It corresponds to computational result of ALU.
- v) Because instruction before the point dataaddress become undefined is J and since there are no data used in j, no value saved in dataaddress.

## Part 1.g

- i) I would have to change aludec module and create a new case in it which gets opcode 000110 which is different than others. Also, I would have to change alu module to get variable value.
- ii) I need to change aludec module and alu module to create a new case. Then, in the case of alu module, I need to do opposite of srl, shifting left instead of right.
 
## Part 2

```
sw+: IM[PC]
   DM[RF[rs]+SignExt(Imm16)] <= RF[rt]
   RF[rs] <= RF[rs]+4
   PC <= PC + 4</pre>
```



Instruction Opcode RegWrite		RegDst	ALUSrcA	ALUSrcB	Branch	MemWrit MemToRe ALU			Jump	
							e	g	Op	
R-type	000000	1	01	0	0	0	0	00	10	00
srl	000000	1	01	1	0	0	0	00	10	00
lw	100011	1	00	0	1	0	0	01	00	00
sw	101011	0	X	0	1	0	1	XX	00	00
beq	000100	0	X	0	0	1	0	01	01	00
addi	001000	1	00	0	1	0	0	00	00	00
j	000010	0	X	X	X	X	0	XX	XX	01
jal	000011	1	10	X	X	X	0	10	XX	01
jr	000000	1	01	0	0	0	0	00	10	10
sw+	001100	1	11	0	1	0	1	11	00	00